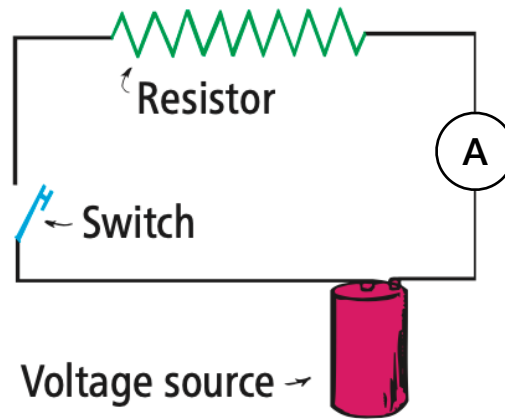


Ch. 23 HW Electric Current


Show **ALL WORK**. You may be randomly selected to solve one of the problems next class which will count towards 20% of your final grade.

- 1) **(5 pts)** A simple electrical circuit consists of a resistor ($6\ \Omega$, ohms), connected to a 12-V battery. An ammeter is placed on the right wire to measure current flow at the specified point




- (a) **(1 pts)** what is the current flow through the circuit on an open switch
- (b) **(3 pts)** if the switch is closed, will current flow? if so, calculate (i) the current that flows through the circuit and (ii) calculate the power consumed by the battery
- (c) **(1 pts)** calculate the current flow if the resistance is *doubled*

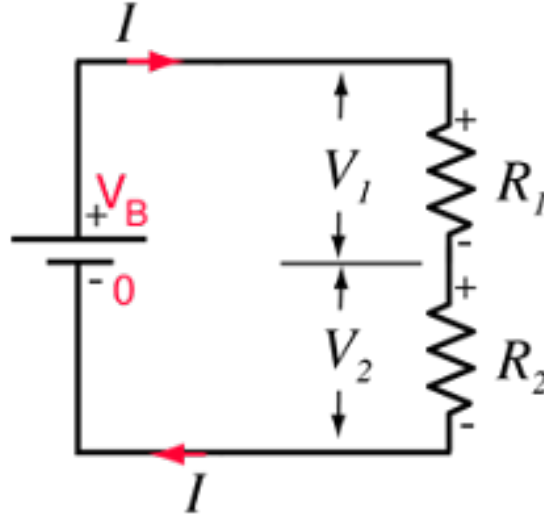- 2) **(20 pts)** An electrical circuit consists of two resistors of resistance $R_1 = 2\ \Omega$ and $R_2 = 4\ \Omega$ connected in *series* to a 12-V battery.



- (a) **(5 pts)** calculate the equivalent resistance, R_{eq}
- (b) **(5 pts)** calculate the total current I across the electrical circuit
- (c) **(5 pts)** calculate the voltage drop V_1 across the first resistor; the voltage drop V_2 across the second resistor and verify that the total voltage drop ($V_1 + V_2$) is 12 Volts.
- (d) **(5 pts)** calculate the power dissipated by each resistor

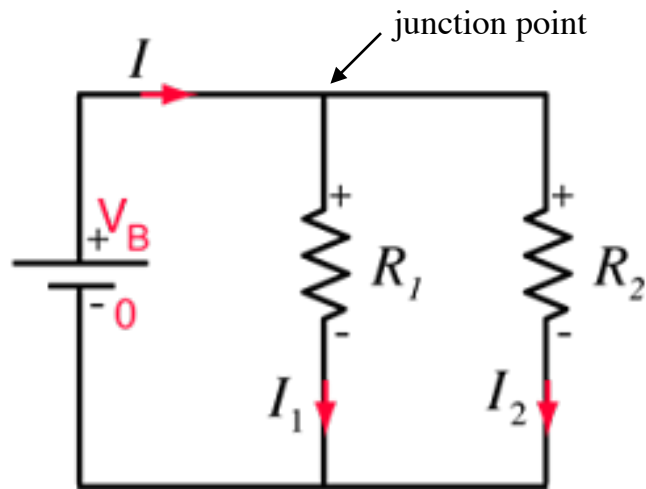- 3) **(20 pts)** An electrical circuit consists of two resistors of resistance $R_1 = 2 \, \Omega$ and $R_2 = 4 \, \Omega$ connected in *parallel* to a 12-V battery.



- (a) **(5 pts)** calculate the equivalent resistance, R_{eq}
- (b) **(5 pts)** what is the voltage drop across each resistor ?
- (c) **(5 pts)** calculate the currents I_1 and I_2 across each resistor
(*hint: apply Ohm's law independently across each resistor to determine the corresponding current*)
- (d) **(5 pts)** calculate the power dissipated across each resistor

4) **(10 pts)** The rate at which electric energy is converted into another form (e.g., mechanical energy, heat, light) is **electric power** ($P = IV$), where power (unit: watts (W) or energy per unit time, J/s). For practical matter, the power company charges its users for energy consumption, in units of kWh (kilowatt-hour), where 1 kWh is the amount of energy transferred in 1 hour at a rate of 1 kW. (*hint: study checkpoint example in section 23.7 of textbook*)

(a) **(5 pts)** If the electric company charges 10 cents / kWh, this means that a 1 kW device operated for 1 hour will cost the user 10 cents. What would be the cost to operate a 1200-W hair dryer for 2 hours ?

(b) **(5 pts)** If the electric company charges 15 cents / kWh, then a 1000-W iron, for example, can operate for 1 hour at a cost of 15 cents. What would be the monthly cost for using the iron if it is operated for 1 hour each week of the month ?